
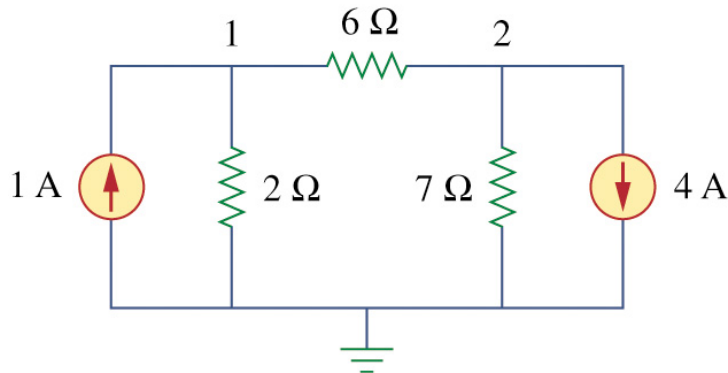


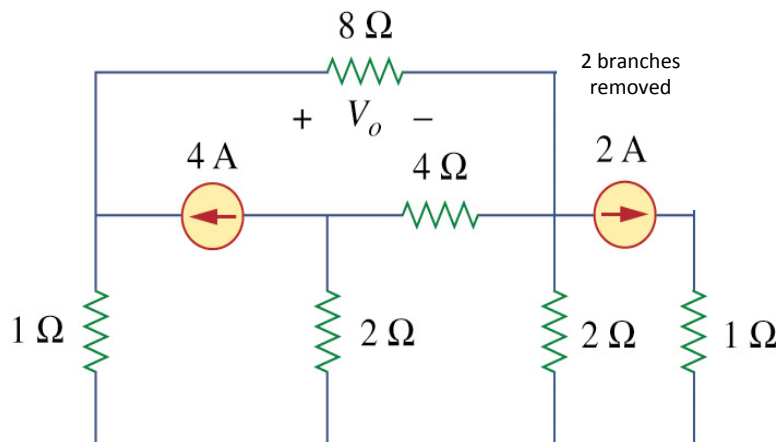1.

Obtain the node voltages in this circuit using nodal analysis by inspection. Remember that the coefficients in the matrix are *conductances*, not *resistances*. Use MATLAB to solve for the node voltage values.




2: Use nodal analysis by inspection and then find V_o in the following circuit (updated 2/9/2017).




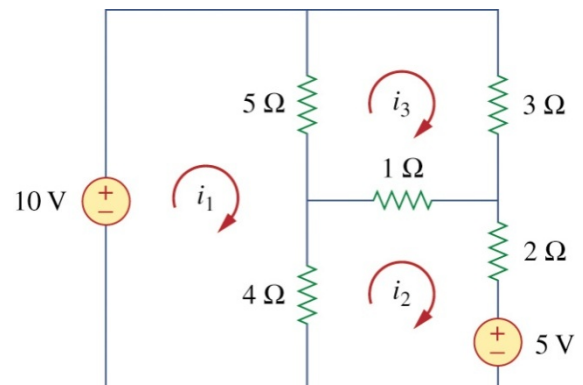3.


Obtain the matrix equation for the mesh currents in the circuit at the right by inspection, then solve for the mesh currents using MATLAB.



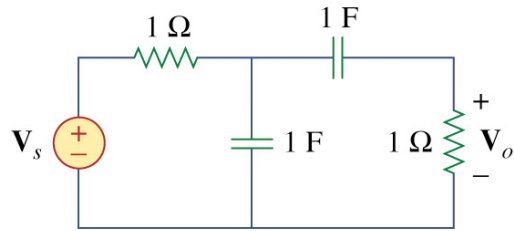4. Determine the center frequency and the bandwidth of the frequency selective circuits in the following figure. You may use inspection techniques if you wish. Treat $\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ and apply the condition for resonance.



(a)

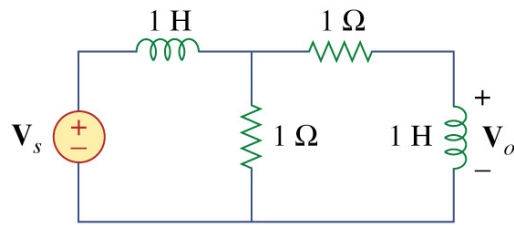

(b)